


# Combinational Logic Circuits

ENCE260: Computer Architecture Topic 7

# Recap


- Each byte in memory has its own address, which is transmitted on the address bus.

	Byte 0								
Address	Bit 0	Bit 1	Bit 2	Bit 3	Bit 4	Bit 5	Bit 6	Bit 7	
0000									Word 0
0001									Word 1
N									Word N

 
 
# Recap

- The ALU performs arithmetic operations and logic comparisons, but only sends the result of one operation at a time to its output.



# Challenge

- What sort of hardware do we need to translate the values on the address bus to a single word-specific activation signal?
- How can we select which ALU operation's result is sent to the ALU output?

# Combinational Logic Circuits

ENCE260: Computer Architecture Topic 7


Selected diagrams from Tocci, Widmer & Moss: Digital Systems

# Common Combinational Logic Circuits

- Decoders & Encoders
- Multiplexers & Demultiplexers
- Multibit Adders
- Multifunction Logic
 
# Decoder

- Typically used for *selecting* a memory location given an address:
- $N$  address bits  $\rightarrow 2^N$  locations
- We want a separate output to be high for each possible combination of inputs.



# Decoder

- 2-to-4 Decoder

Code Input	$A_1$ $A_0$		$D_0$ $D_1$ $D_2$ $D_3$				Decoded Output
	0	0	1	0	0	0	
	0	1	0	1	0	0	
	1	0	0	0	1	0	
	1	1	0	0	0	1	



# Decoder


- 2-to-4 Decoder

Code Input	$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$	Decoded Output
	0	0	1	0	0	0	
	0	1	0	1	0	0	
	1	0	0	0	1	0	
	1	1	0	0	0	1	

$$\begin{aligned}
 D_0 &= \overline{A_1} \overline{A_0} & D_2 &= A_1 \overline{A_0} \\
 D_1 &= \overline{A_1} A_0 & D_3 &= A_1 A_0
 \end{aligned}$$

# Decoder

- 2-to-4 Decoder

 

$$D_0 = \overline{A_1} \overline{A_0}$$

$$D_1 = \overline{A_1} A_0$$

$$D_2 = A_1 \overline{A_0}$$

$$D_3 = A_1 A_0$$

# Decoder

- 2-to-4 Decoder



SN74LVC1G139

SCES602E – AUGUST 2004 – REVISED JANUARY 2018

## SN74LVC1G139 2-to-4 Line Decoder


### 1 Features

- Available in the Texas Instruments NanoStar™ and NanoFree™ Packages
- Supports 5-V  $V_{CC}$  Operation
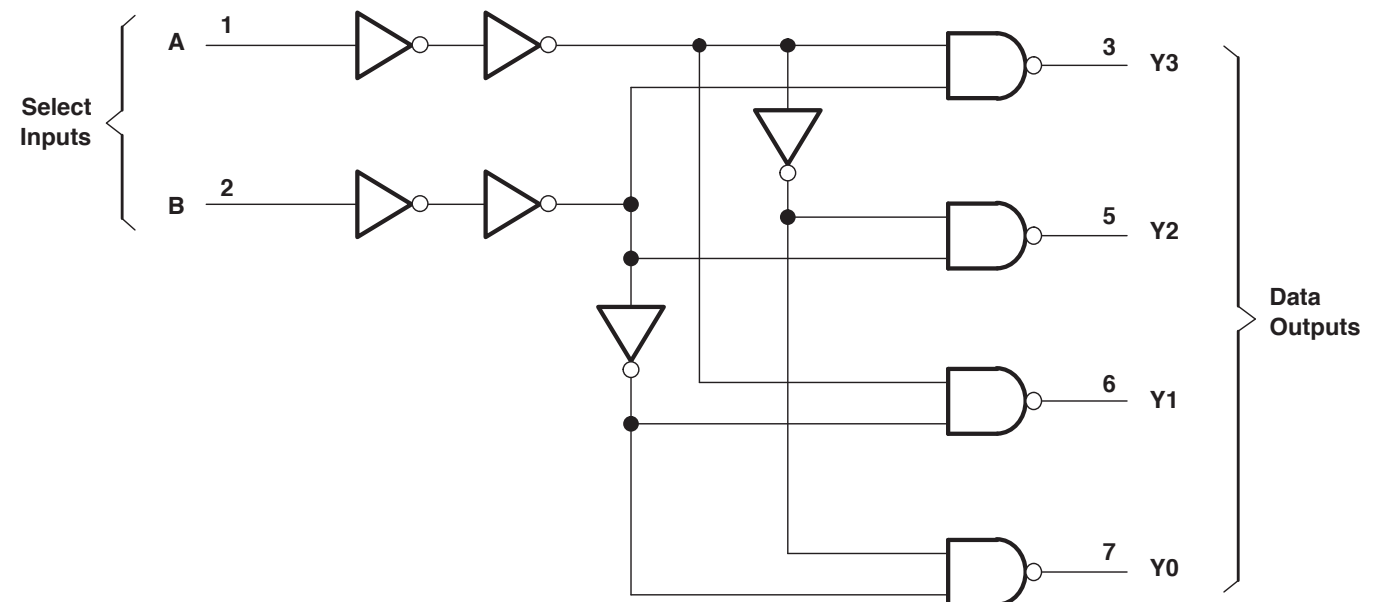
### 3 Description

This SN74LVC1G139 2-to-4 line decoder is designed for 1.65-V to 5.5-V  $V_{CC}$  operation.

The SN74LVC1G139 2-line to 4-line decoder is



# Decoder

- 2-to-4 Decoder



SN74LVC1G139

SCES602E – AUGUST 2004 – REVISED JANUARY 2018

## SN74LVC1G139 2-to-4 Line Decoder


### 1 Features

- Available in the Texas Instruments NanoStar™ and NanoFree™ Packages
- Supports 5-V  $V_{CC}$  Operation
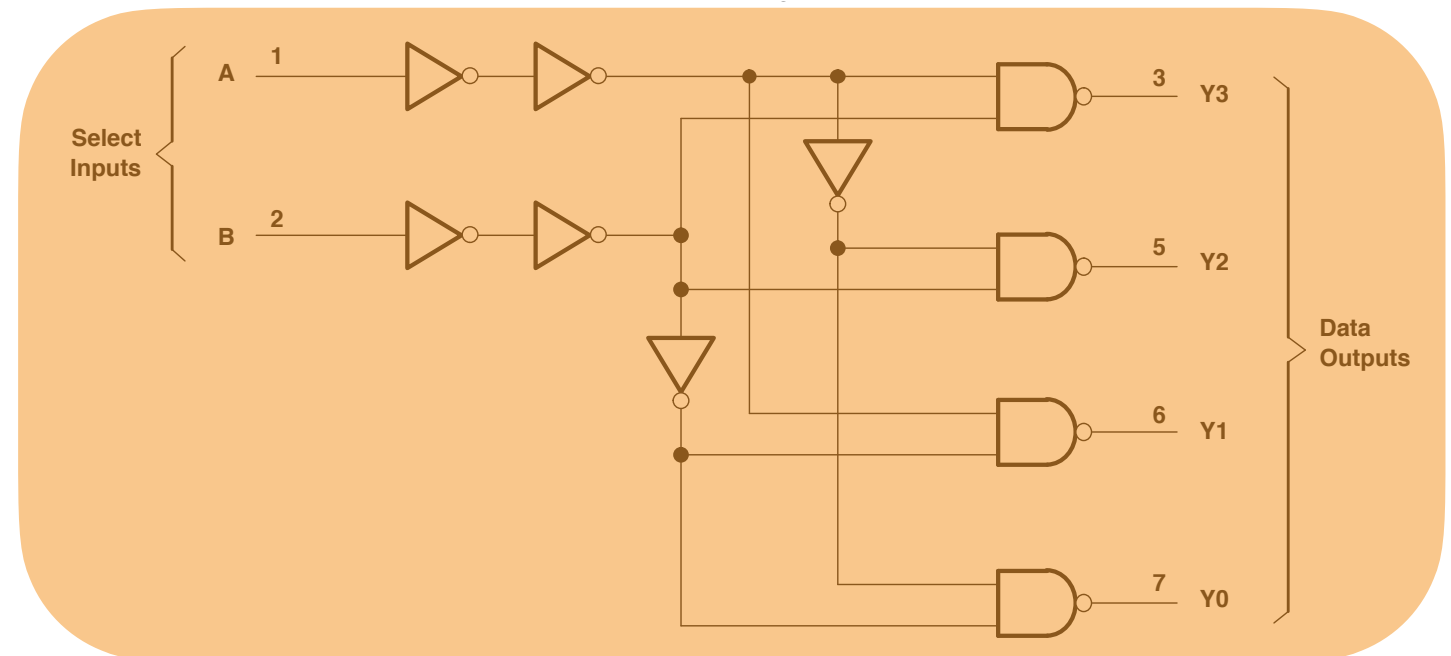
### 3 Description


This SN74LVC1G139 2-to-4 line decoder is designed for 1.65-V to 5.5-V  $V_{CC}$  operation.

The SN74LVC1G139 2-line to 4-line decoder is



# Decoder

- 3-to-8 Decoder

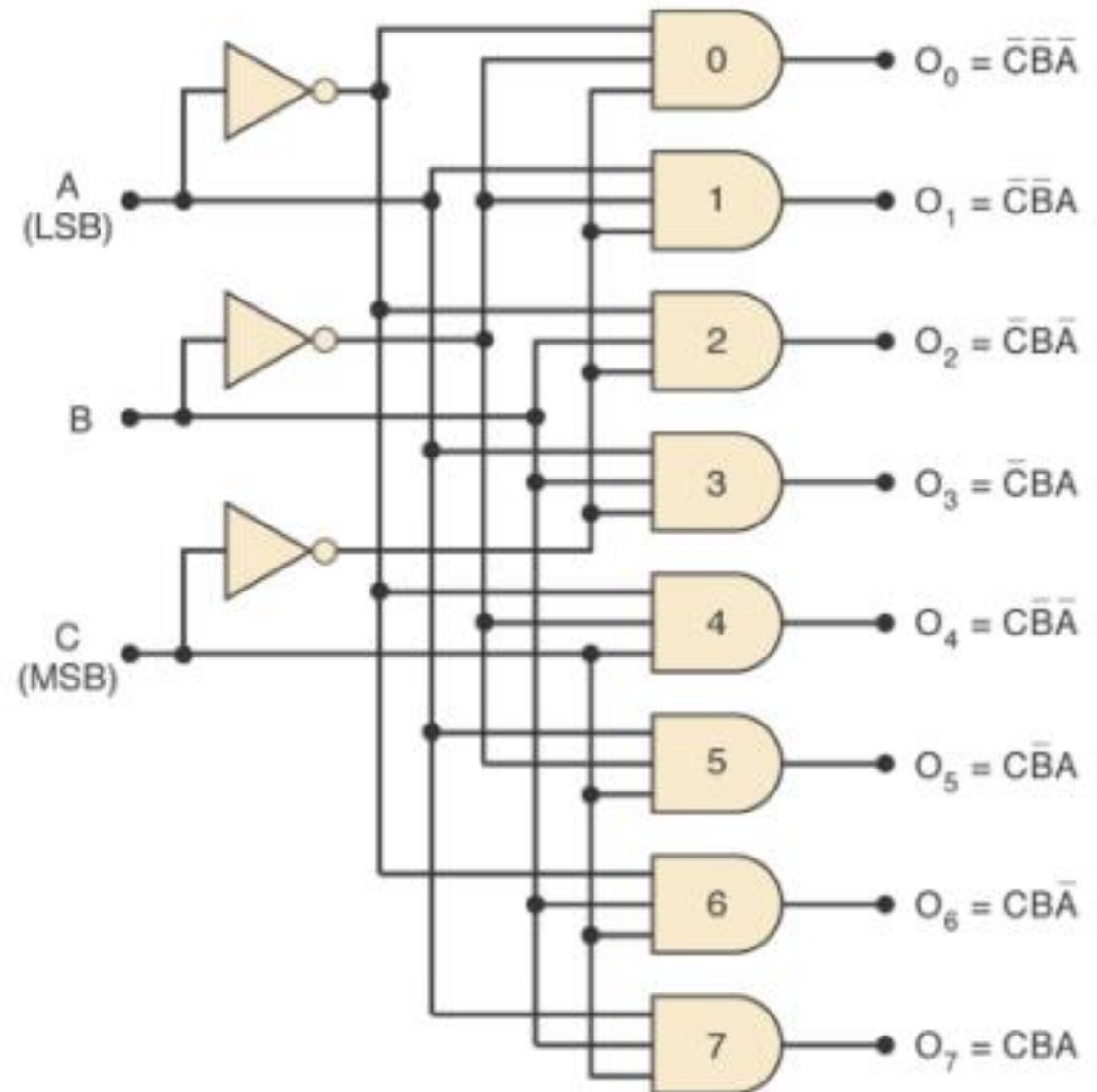


# Encoder

Raw  
Input

$D_0$	$D_1$	$D_2$	$D_3$	$A_1$	$A_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1


Encoded  
Output

 

Tutorial: what would  
the logic circuit look like  
for this device?

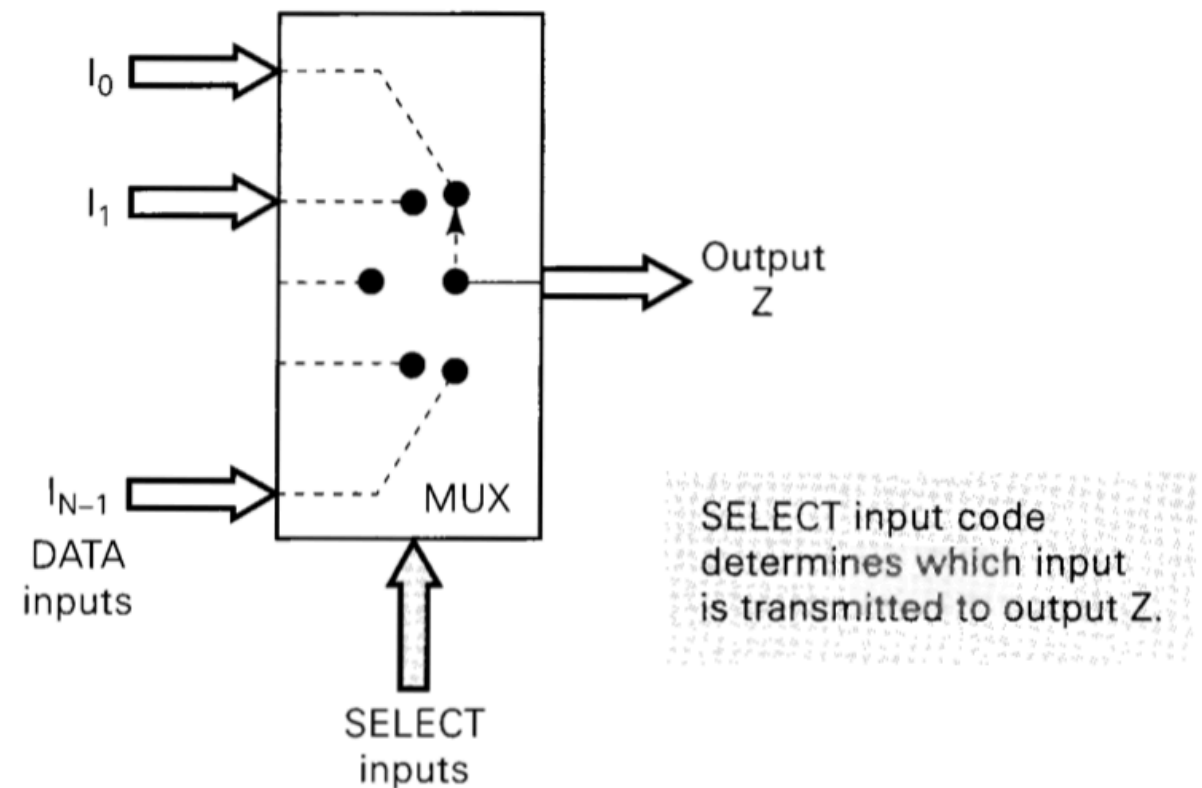
# Multiplexer

- Multiplexers (muxes) select one or more of several inputs and send them to the output.
- N-to-1 muxes are most common, but can also get N-to- $N/2$  or N-to- $N/4$  muxes.



# Multiplexer

- 2:1 Multiplexer

 


Input			Output
$S$	$I_1$	$I_2$	$O$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



# Multiplexer

- 2:1 Multiplexer

 


Input $S$	Output $O$
0	$I_0$
1	$I_1$

$$O = \overline{S}I_0 + SI_1$$


# Multiplexer

- 2:1 Multiplexer

 

 
# Example: ALU

- ALUs can perform arithmetic calculations as well as logical comparisons.
- In practice, they do both a calculation and a comparison on every pair of inputs they are given.
- A mux is used to determine whether the arithmetic or logical result is sent to the output.



# Example: ALU

 


Function Table

S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Operation	Comments
0	0	0	CLEAR	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 0000
0	0	1	B minus A	} Needs C <sub>N</sub> = 1
0	1	0	A minus B	
0	1	1	A plus B	Needs C <sub>N</sub> = 0
1	0	0	A ⊕ B	Exclusive-OR
1	0	1	A + B	OR
1	1	0	AB	AND
1	1	1	PRESET	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 1111

Notes: S inputs select operation.  
OVR = 1 for signed-number overflow.

 A = 4-bit input number  
B = 4-bit input number  
C<sub>N</sub> = carry into LSB position  
S = 3-bit operation select inputs  
F = 4-bit output number  
C<sub>N+4</sub> = carry out of MSB position  
OVR = overflow indicator



# Multiplexer

- Tutorial:
  - Carry out the design process (truth table, logic expression and circuit diagram) for a 4:1 multiplexer.
  - Combine two 2:1 multiplexers to make a 4:2 multiplexer.

# Demultiplexer

- Conceptually similar to a mux, but with swapped inputs and outputs.
- I:4 Demux

Inputs			Outputs			
$I$	$S_1$	$S_2$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	X	X	0	0	0	0




# Adder

- We have already seen a full adder circuit that adds two 1-bit numbers, with carry in and carry out.
- We have also seen how to do binary addition on 4-bit 2's complement numbers (Tute 2).
- ALUs combine  $N$  1-bit full adders, where  $N$  is the word length of the processor.

# 1 -Bit Adder





## Full Adder

 



# 3-Bit Adder



## Full Adder

    

## 3-Bit Ripple Carry Adder

# 3-Bit Adder



## Full Addder

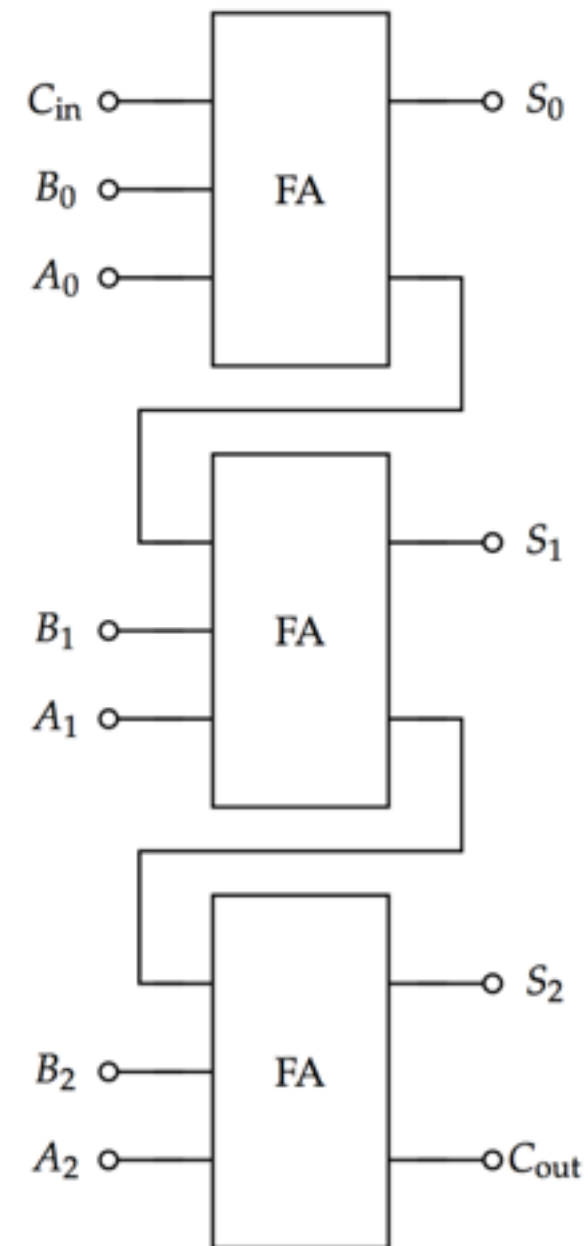 

## 3-Bit Ripple Carry Adder

# 3-Bit Adder

## Full Adder

  

## 3-Bit Ripple Carry Adder

# Subtraction

- *We could* design a circuit to perform binary subtraction, e.g.  $3 - 4 = ?$
- Instead, we use the properties of 2's complement encoding and our adder circuitry, since  $3 - 4 = 3 + (-4)$ .

# Subtraction

minuend 3 – 4 = -1 difference  
subtrahend

- To perform a subtraction, convert the subtrahend to a 2's complement negative number:

	0	1	0	0	= +4
	1	0	1	1	1's complement
+	0	0	0	1	add 1
	1	1	0	0	= -4

- Then add the result to the minuend:

	0	0	1	1	
+	1	1	0	0	
	1	1	1	1	= -1

# Subtraction

- So how do we implement a 2's complement negative conversion using digital logic?
- 1's complement:

Inputs		Output
<i>Sub?</i>	<i>In</i>	<i>Out</i>
0	0	0
0	1	1
1	0	1
1	1	0

# Subtraction

- So how do we implement a 2's complement negative conversion using digital logic?

- 1's complement:

$$Out = Sub \oplus In$$

Inputs		Output
<i>Sub?</i>	<i>In</i>	<i>Out</i>
0	0	0
0	1	1
1	0	1
1	1	0


# Subtraction

- So how do we implement a 2's complement negative conversion using digital logic?
- 1's complement:
- Add 1:  $C_{in} = 1$ .

Inputs		Output
<i>Sub?</i>	<i>In</i>	<i>Out</i>
0	0	0
0	1	1
1	0	1
1	1	0




# Subtraction

 

# Multifunction Logic

- When is an AND gate not an AND gate?

 

		s <sub>1</sub>		
		0	1	1
		1	0	1
Inputs		Output O		
a	b	AND	OR	XOR
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0

# Multifunction Logic




SN74LVC1G99

www.ti.com

SCES609G – SEPTEMBER 2004 – REVISED NOVEMBER 2013

## Ultra-Configurable Multiple-Function Gate With 3-State Output

Check for Samples: [SN74LVC1G99](#)

 

NO. OF INPUTS	AND/NAND FUNCTION	OR/NOR FUNCTION	$\overline{OE}$	A	B	C	D
2	3-state AND	3-state NOR, both inputs inverted	L	L	Input 1	Input 2	L

# Summary

- Combinational devices like muxes, encoders and adders are like high-level constructs in a programming language: they allow us to implement sophisticated functionality with minimal effort.